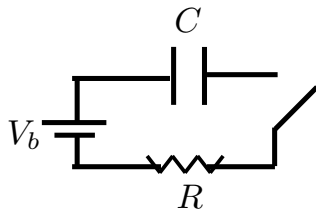


RC Circuits:

- Lets look at a circuit that has **both** a capacitor and a resistor in series with a voltage source:



- Suppose the circuit has a switch that is initially open.
- The capacitor has no net charge on its plates.
- Since the circuit is broken, charge cannot move: $I(0) = \frac{dq}{dt} = 0$
- Once the switch is closed, charge will build up on the capacitor until $q_{max} = CV$

- What is the charge on the capacitor as a function of time when the switch is closed?

- We have only one loop, so Kirchoff #1 is trivial.
- Using Kirchoff #2:

$$V_b - V_C - V_R = V_b - \frac{q(t)}{C} - R \frac{dq(t)}{dt} = 0$$

- This can be turned into a 1st-order differential equation:

$$\frac{dq(t)}{dt} + \frac{q(t)}{RC} = \frac{V_b}{R}$$

146

- The solution to this equation can be guessed (see pg. 850 of your text), however I will show you how to solve this equation on this slide:

- We have the equation: $q'(t) + \frac{1}{RC}q(t) = V_b/R$

- Take the stuff multiplying $q(t)$, and solve $e^{\int \frac{1}{RC} dt} = e^{\frac{t}{RC}}$

- Multiply both sides by this result:

$$e^{\frac{t}{RC}} q'(t) + e^{\frac{t}{RC}} \frac{1}{RC} q(t) = V_b/R e^{\frac{t}{RC}}$$

- The left-hand side now simplifies to: $\frac{d}{dt} \left[e^{\frac{t}{RC}} q(t) \right] = \frac{V_b}{R} e^{\frac{t}{RC}}$

- Integrating we get: $e^{\frac{t}{RC}} q(t) = CV_b e^{\frac{t}{RC}} + C_1$ where C_1 is an integration constant

- At $t=0 \rightarrow q=0$ therefore $C_1 = -CV_b$ and:

$$q(t) = CV_b \left[1 - e^{-t/RC} \right] \quad CV_b = q_{max} \quad \longrightarrow \quad q(t) = q_{max} \left[1 - e^{-t/RC} \right]$$

147

- Either by guessing, or solving the equation for $q(t)$, we get:

$$q(t) = q_{\max} \left[1 - e^{-t/RC} \right]$$

- When $t=0 \rightarrow q=0$ and when $t \gg RC \rightarrow e^{-t/RC} \approx 0$ and $q=q_{\max}$.
- It is typical to combine R and C into a single number with units of time

$RC = \tau$ **Time Constant** of the circuit

$$q(t) = q_{\max} \left[1 - e^{-t/\tau} \right]$$


- We can also easily solve for the current by differentiating $q(t)$:

$$I(t) = \frac{q_{\max}}{\tau} e^{-t/\tau} = \frac{q_{\max}}{RC} e^{-t/RC} = \frac{V_b}{R} e^{-t/RC}$$

- For $t \gg RC$, the current is nearly zero as the capacitor has built up all the charge it can store
- When $t = \tau$: $I = \frac{1}{e} \frac{V_b}{R}$ - Time constant tells you how long it takes for current to drop by $1/e$.

148

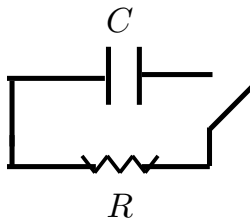- What if we start with a charged capacitor and no voltage source?



- At $t=0$ we close the switch as current starts to flow
- Want to know what $q(t)$ and $I(t)$ are
- Using Kirchhoff voltage law: $-IR - V_C = 0$

- The equation of motion for charge is: $\frac{dq(t)}{dt} + \frac{q(t)}{RC} = 0$

- Equation is similar to previous case, but will have no integration constant remaining.


- Try exponential solution for q : $q(t) = Ae^{-t/RC}$

- Arrive at $q(t) = q_{\max} e^{-t/RC}$

- And differentiating: $I(t) = -\frac{q_{\max}}{RC} e^{-t/RC}$

149

ex. RC Circuits:

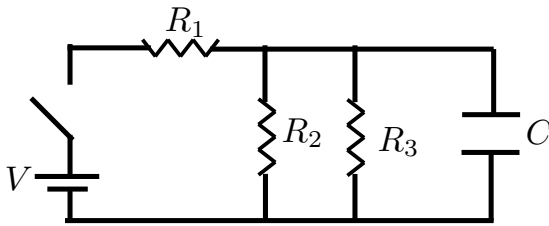


1) Determine potential across capacitor after switch has been closed for a long time.

2) Determine the energy stored in the capacitor after a long time.

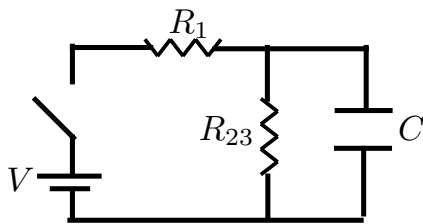3) After switch is closed, how much energy is dissipated in R3?

- Obviously R2 & R3 are in parallel, so the circuit can be simplified to:



$$R_{23} = \frac{R_2 R_3}{R_2 + R_3}$$


- Since R23 & C are in parallel, the voltage across them is the same.



Can find V_C by calculating: $V_{23} = I_{23} R_{23}$

150

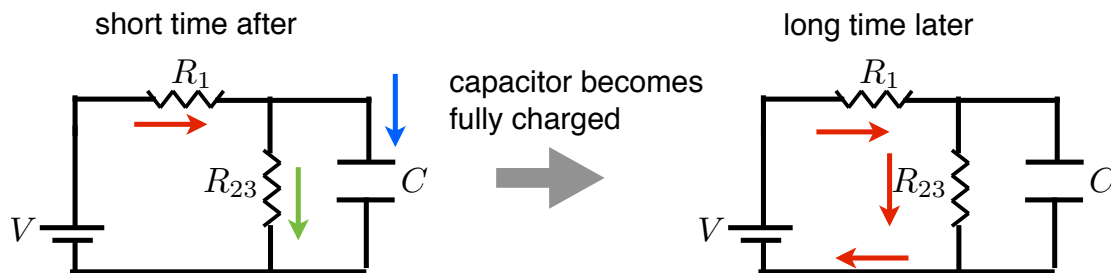- Need to find the current through R23 after switch has been closed for a long time



- Once capacitor is fully charged no current can flow through it

$$I_{23} = \frac{V}{R_1 + R_{23}}$$



$$V_C = V_{R_{23}} = I_{23} R_{23} = \frac{V R_{23}}{R_1 + R_{23}}$$

-Now need to find the energy stored in the capacitor at late time:

$$U = \frac{1}{2} C V_C^2 = \frac{1}{2} C \left(\frac{V R_{23}}{R_1 + R_{23}} \right)^2$$

151

3) What is the energy dissipated by the resistor R3?

- Resistor is Ohmic so that the power (energy/time) is: $P(t) = \frac{V_{R_3}(t)^2}{R_3} = \frac{V_C(t)^2}{R_3}$

- Therefore by integrating the power we get energy: $E = \int_0^{t_f} \frac{V_C(t)^2}{R_3} dt$

- Since the capacitor is in parallel with R23:

$$V_C(t) = \frac{q(t)}{C} = \frac{CV_C}{C} e^{-t/R_{23}C} = V_C e^{-t/R_{23}C}$$

- Substituting into the power:

$$E = \frac{V_C^2}{R_3} \int_0^\infty e^{-2t/R_{23}C} dt = \frac{R_{23}CV_C^2}{2R_3}$$