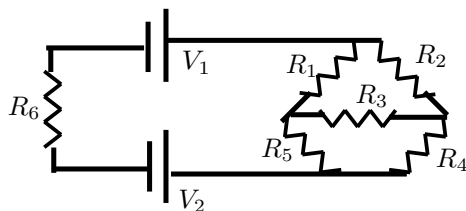


Direct Current Circuits

134

- So far we have dealt with circuits composed of one voltage source, and capacitors and resistors that can be simplified into a single equivalent capacitor or resistor.

- What happens if there is more than one voltage source, or the circuit is too complex to simplify?




- To solve a general circuit requires **Kirchoff's Law's**:

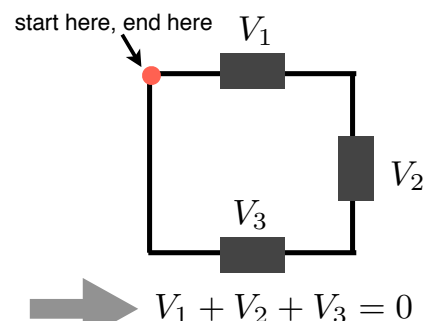(1) $\oint \vec{E} \cdot d\vec{l} = 0$ Potential around any loop = 0


- We have seen this rule already. It comes from the conservative nature of the E-field.

- Some potentials must obviously be negative



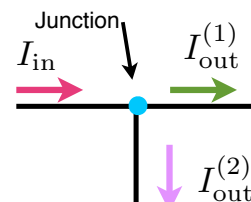
(2) Charge conservation: Charge cannot piled up.

at any junction:
$$I_{\text{in}} = \sum_k I_{\text{out}}^{(k)}$$



135

ex simple circuit:

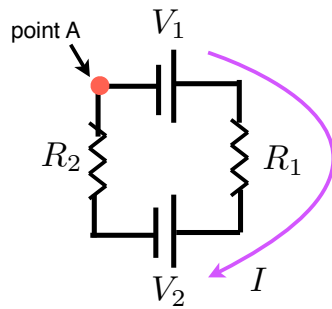

- What is the magnitude and direction of current?

- **Step #1:** Decide the current direction in the circuit loop:

- Direction you pick does not matter
- Once you pick directions, you cannot change
- Now we have already satisfied Kirchoff #2

We will assume current goes clockwise here:

- **Step #2:** Do Kirchoff's 2nd law: $\sum_i V_i = 0$ along any closed loop


- Pick a starting point along the circuit ("point A")
- We must now decide what the sign of the potential will be across each device:

if going from low \rightarrow high potential = + sign

if going from high \rightarrow low potential = - sign

- Go around loop in the same direction as the current goes.

136

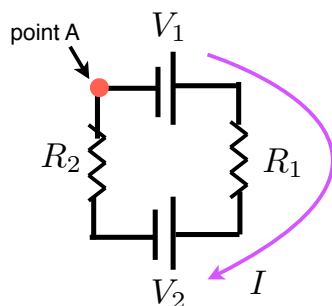

- Start at "A" and go clockwise:

- Potential at V1 goes from low (-) to high(+) therefore potential is +V1

- Next go across R1, potential goes from high to low since current is going in that direction and current is (+)-charges

$$V_{R_1} = -IR_1$$

- Across V2, go from (+) to (-) which means that we get -V2

- R2 is the same as R1, going from high \rightarrow low

$$V_{R_2} = -IR_2$$

- Now use Kirchoff's 2nd law: add up all the potentials and set =0

$$V_1 - IR_1 - V_2 - IR_2 = 0 \quad \longrightarrow \quad V_1 - V_2 = I(R_1 + R_2)$$


- Resistors add up since they are in series (as expected)

- Current I is negative if $V_2 > V_1$ (since $R_1, R_2 > 0$):

If current is negative then it goes in the opposite direction you picked in step #1 (Counter clockwise in this example)


137

ex 2-loop circuit:

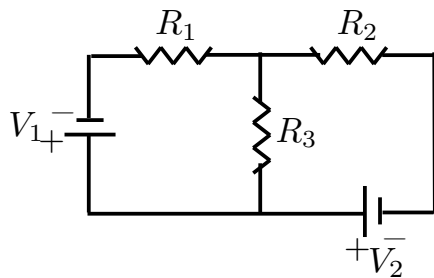

- What is the current I_1 , I_2 , I_3 , through each resistor?
- Want magnitude and direction

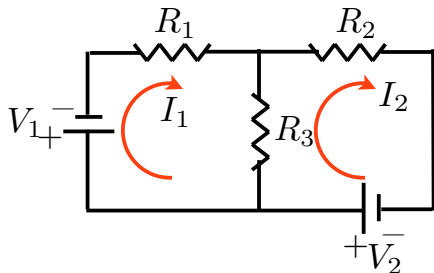- **Step #1:** Decide the direction of current going through each loop.



- There is a different current assigned to each closed loop
- Choose the same direction for each current to make life easy. You just get minus sign if you are wrong.
- Again, we have already satisfied Kirchhoff's Law #1.
- Do not need to define I_3 , we see that I_3 depends on I_1 and I_2


138

- **Step #2 :** Kirchhoff #2

- pick starting point for loop #1 and go around in same direction as current I_1

$$-V_1 - I_1 R_1 - I_1 R_3 + I_2 R_3 = 0$$

I_2 in opposite direction as I_1

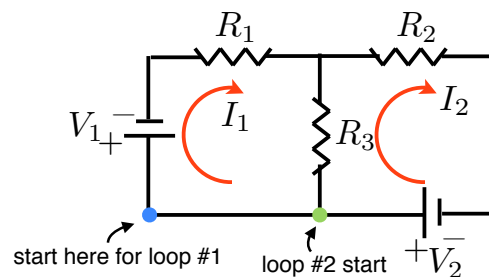

- If current goes in opposite direction that you go around loop, then you must give minus sign to each voltage drop

- do the same for loop #2: $-I_2 R_3 + I_1 R_3 - I_2 R_2 + V_2 = 0$

I_1 in opposite direction as I_2

- Solve for I_1 and I_2 (two equations, two unknowns)


$$I_1 (R_1 - R_3) + R_3 I_2 = V_1$$

$$I_1 R_2 - I_2 (R_3 + R_2) = -V_2$$

139

- If I_1 is positive, then you picked the correct direction:

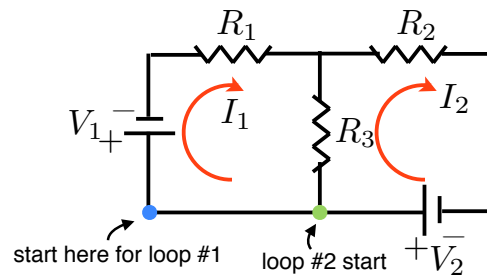- If I_1 is positive:
- If I_1 is negative:



- This solution method is sensitive to the sign (direction) of current

- I_3 can be solved since we know I_1 and I_2 :

- Assume: $I_1 = +3 \text{ A}$ $I_2 = +1 \text{ A}$


$$\Rightarrow I_3 = I_1 - I_2 = 2 \text{ A}$$

since I_2 in opposite direction

- I_3 in same direction as I_1 in this example

140

Ex. Solving Circuits (prob. 26.63):

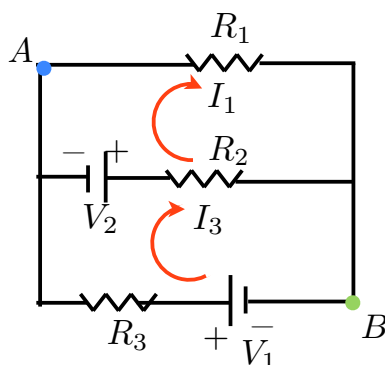

$$R_1 = 10 \, \Omega \quad R_2 = 20 \, \Omega \quad R_3 = 30 \, \Omega$$

$$V_1 = 15 \text{ V} \quad V_2 = 9 \text{ V}$$

Question: What is the power through each of the resistors if the resistors obey Ohm's Law?

- For Ohmic resistors we know: $P = I^2 R$
- Must find the currents flowing through each resistor.

Step #1: Pick the directions for the currents I_1 and I_3

- Current through resistor #2 (I_2) will obviously be a combination of I_1 and I_3

Step #2: Pick a starting point, and go around each loop in the direction of the currents from step #1.

For current #1 (starting at A): $-I_1 R_1 - I_1 R_2 + I_3 R_2 - V_2 = 0$

For current #3 (starting at B): $V_1 - I_3 R_3 + V_2 - I_3 R_2 + I_1 R_2 = 0$

141

- We are left with two equations and two unknown variables (I_1 & I_3)
- We could solve the equation for current #1 to get I_1 in terms of I_3 and other given variables, and then plug into the equation for current #3.
- This gets kind of messy, so we will use **Cramer's Rule** instead:
- Lets write our system of equations in matrix form:

$$\begin{bmatrix} -(R_1 + R_2) & R_2 \\ R_2 & -(R_2 + R_3) \end{bmatrix} \begin{bmatrix} I_1 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_2 \\ -(V_1 + V_2) \end{bmatrix}$$

- Plug in values for resistors and voltages:

$$\begin{bmatrix} -30 & 20 \\ 20 & -50 \end{bmatrix} \begin{bmatrix} I_1 \\ I_3 \end{bmatrix} = \begin{bmatrix} 9 \\ -24 \end{bmatrix}$$

Going to call this matrix M

142

- Need to find the determinant of matrix M

$$M = \begin{bmatrix} -30 & 20 \\ 20 & -50 \end{bmatrix} \quad \det M = (-30 \times -50) - (20 \times 20) = 1100$$

- Cramer's rule says I_1 can be found by replacing the first column of M with the RHS voltage values and dividing by the det M

$$I_1 = \frac{\det \begin{bmatrix} 9 & 20 \\ -24 & -50 \end{bmatrix}}{\det M} = \frac{30}{1100} = \frac{3}{110}$$

$I_1 = \frac{3}{110} \text{ A}$

- To find I_3 , replace the second column of M, and repeat:

$$I_3 = \frac{\det \begin{bmatrix} -30 & 9 \\ 20 & -24 \end{bmatrix}}{\det M} = \frac{540}{1100} = \frac{54}{110}$$

$I_3 = \frac{54}{110} \text{ A}$

- Since $I_3 > I_1$, the current I_2 is simply $I_3 - I_1$:

$I_2 = I_3 - I_1 = \frac{54}{110} - \frac{3}{110} = \frac{51}{110} \text{ A}$

143

- Having found the currents, the power is easy to evaluate:

$$P_1 = I_1^2 R_1 = 0.0074 \text{ W}$$

$$P_2 = I_2^2 R_2 = 4.30 \text{ W}$$

$$P_3 = I_3^2 R_3 = 7.23 \text{ W}$$

- To double check our answers, at point C, $I_1 + I_2 = I_3$ by Kirchoff #2 **OK!**


- The potential drop from the left side of the circuit to the right is the same along each branch. Verify the potential is the same across each branch:

Top: $V = -I_1 R_1 = -0.2727 \text{ V}$

Middle: $V = 9 - I_2 R_2 = -0.2727 \text{ V}$

Bottom: $V = R_3 I_3 - V_1 = -0.2727 \text{ V}$

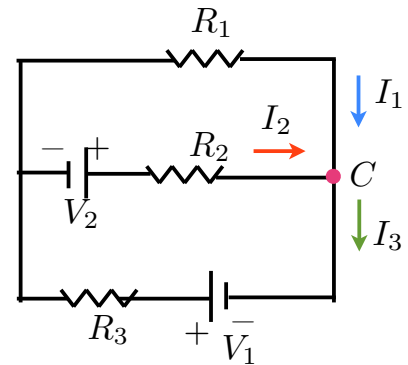↪ sign changes here since I_3 goes right→left and we go left→right




144

Ammeters & Voltmeters

- Now that we are able to calculate the currents and voltages in circuits, we would like to compare our results with the actual values obtained from experiment

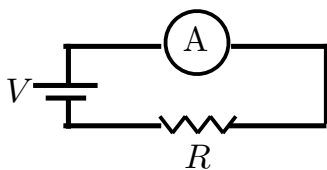- To measure how much current is flowing through a particular part of the circuit we use an **ammeter**:




- The ammeter must be in the circuit loop so the current goes through the ammeter.

- Ammeters have very low resistance so that they do not change the value of the current.

$$V = IR \rightarrow I = V/R$$

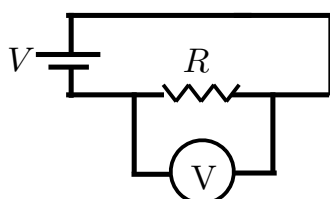- To measure the voltage (potential) across a circuit element, we use a **voltmeter** in parallel:



- The ends of the voltmeter must be on opposite sides of the circuit element since only potential differences matter

- Voltmeters have extremely high resistance so almost no current flows through them.

145