

- We have shown that the maximum current occurs on resonance, but what about if we use a different frequency while keeping R, L, and C fixed?

$$I_{\max} = \frac{V_0}{Z} \quad Z = \sqrt{R^2 + X^2} = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

### First Case:

$$\omega \rightarrow 0, Z \rightarrow \infty \rightarrow I_{\max} \rightarrow 0$$

- Due to the capacitor

- As the frequency  $\rightarrow 0$ , the current is no longer AC but DC. DC-current builds up charge on the capacitor until no more current can flow.


### Second Case:

$$\omega \rightarrow \infty, Z \rightarrow \infty \rightarrow I_{\max} \rightarrow 0$$

- Due to the inductor


- If frequency is very high then current changes extremely rapidly. Self-inductor tries really hard to fight rapid changes in current that generate rapid B-field changes

222

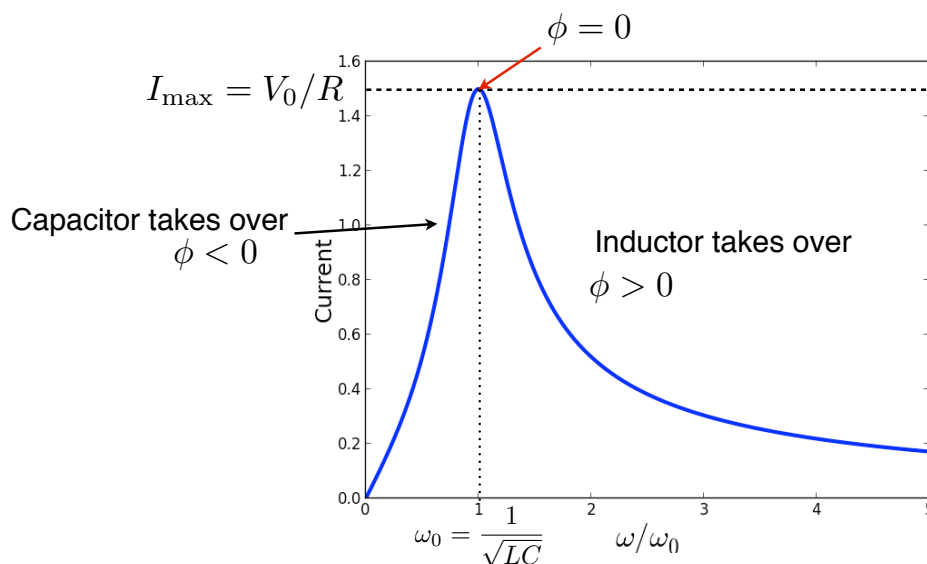
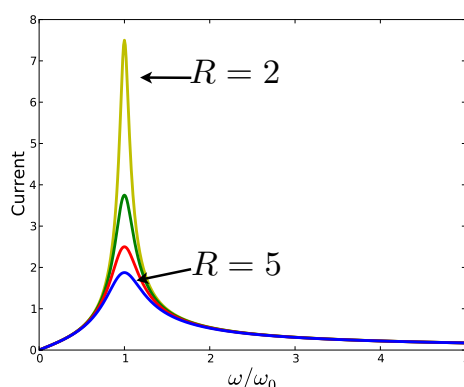
### Parameters

$V = 7.5 \text{ V}$   
 $R = 5 \Omega$   
 $L = 8.2 \text{ mH}$   
 $C = 100 \mu\text{F}$



- What happens if R is decreased?

- The width of the peak decreases and the maximum current increases rapidly.

- If resistance is too low, can destroy your circuit if driving frequency is on resonance.


223

- We want some numerical way to describe the width of the peak at the resonance frequency

- This is called the **Quality Factor**:

$$Q = \frac{\omega_0}{\Delta\omega}$$

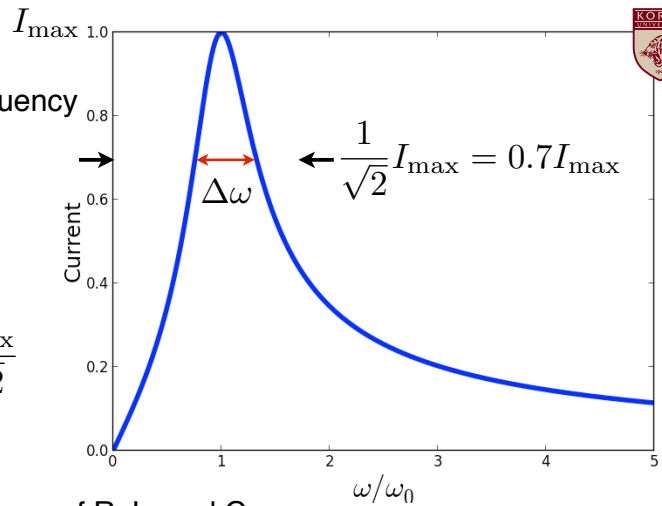-  $\Delta\omega$  is the width of the peak at  $I = \frac{I_{\max}}{\sqrt{2}}$



- The quality factor can also be written in terms of R, L, and C.


$$Q = \frac{\omega_0}{\Delta\omega} = \frac{1}{\sqrt{LC}} \frac{L}{R} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

- The quality factor tells us how strongly the system behaves on resonance, and how weakly it responds when not on resonance.

- Because  $Q \sim 1/R$ , the Q-factor also tells us how much energy is lost during each period T.

224

### Ex. Metal Detector:

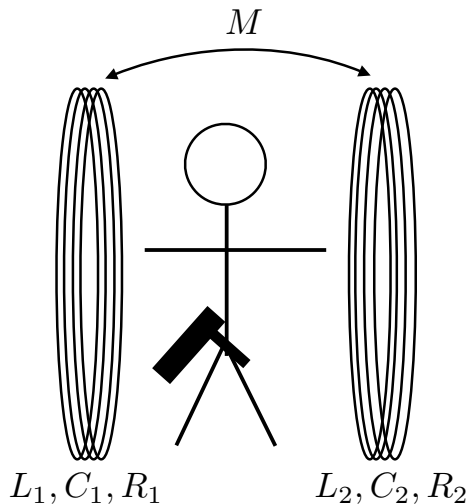



- Metal detector is made from two-coupled LRC Oscillators

- Coupled via mutual inductance (haven't discussed this in detail)

- Two different resonance peaks (just going to show one)

- Oscillators have extremely large Q-factors (i.e. very sensitive to change in frequency)

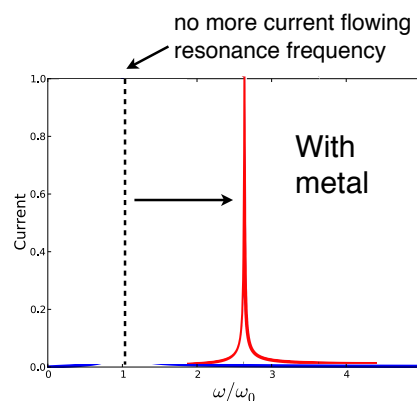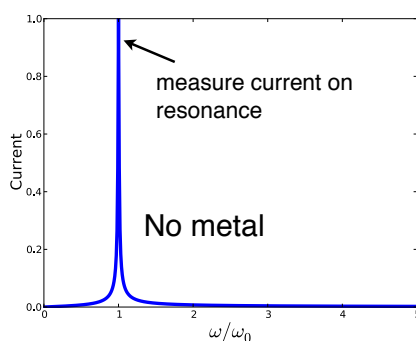- Eddy currents generated in metal, generated B-field that shifts resonance frequency



225

## Power in AC-Circuits:

- Why did we define the Q-factor as the width at  $I = \frac{I_{\max}}{\sqrt{2}}$  and not  $I = \frac{I_{\max}}{2}$  ?
- In the real-world we are not interested in the current, but rather the power  $P \propto I^2$

$$P = I^2 R = [I_{\max} \cos(\omega t - \phi)]^2 R = I_{\max}^2 R \cos^2(\omega t - \phi)$$

- The current oscillates in time, so let's calculate the average power using:

$$\langle I \rangle = \frac{1}{\sqrt{2}} I_{\max} \quad \text{Average over one-period} \rightarrow \langle P \rangle = \frac{1}{2} I_{\max}^2 R$$

- It is also common to define the **RMS (Root-Mean-Squared) Current**:  $I_{\text{rms}} = \frac{1}{\sqrt{2}} I_{\max}$

$$\rightarrow \boxed{\langle P \rangle = I_{\text{rms}}^2 R} \quad \text{- In AC-circuits, when people talk about current, they always mean the RMS current.}$$


- We can also define the **RMS Voltage**:  $V_{\text{rms}} = V_{\max}/\sqrt{2}$

$$\rightarrow \boxed{I_{\text{rms}} = \frac{V_{\text{rms}}}{Z}}$$

226

- The average power can now be expressed using RMS values for both the current and the voltage:
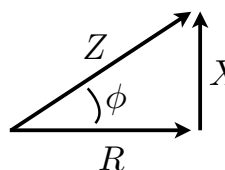
$$\langle P \rangle = I_{\text{rms}}^2 R = \frac{V_{\text{rms}}}{Z} I_{\text{rms}} R = \boxed{I_{\text{rms}} V_{\text{rms}} \frac{R}{Z}}$$



$$\rightarrow \frac{R}{Z} = \cos \phi \rightarrow \langle P \rangle = I_{\text{rms}} V_{\text{rms}} \cos \phi$$

227