
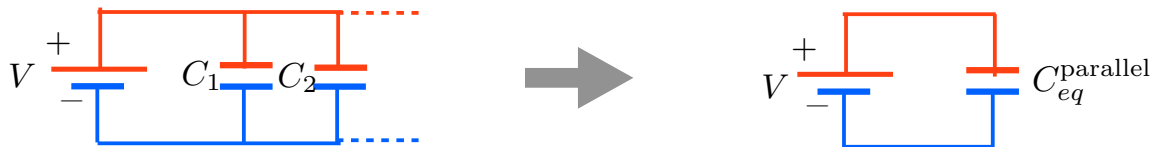


- Recall from last time:

Voltage across each C is the same

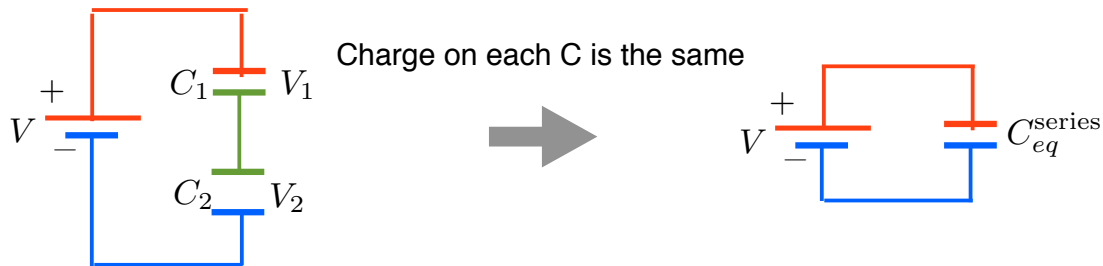

Equivalent capacitance given by: $C_{eq}^{parallel} = \sum C_i^{parallel}$




Equivalent capacitance given by: $\frac{1}{C_{eq}^{series}} = \sum \frac{1}{C_i^{series}}$

- Can use these to simplify a collection of capacitors into a single equivalent capacitor

105

Ex. Simplifying Capacitors I:

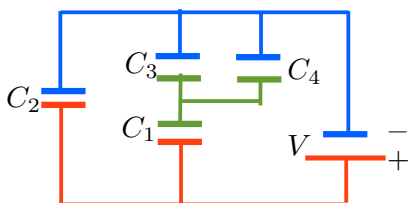

- Want to reduce problem to single capacitor. What is the equivalent capacitance?

- Want to reduce problem to single capacitor. What is the equivalent capacitance?

- Need to begin with C3 and C4. Cannot do C1 and C3 first since C4 is connected in the middle.


$$C_{eq}^1 = C_3 + C_4$$

- Now we need to do the capacitors in series since nothing is in parallel at the moment

$$\frac{1}{C_{eq}^2} = \frac{1}{C_1} + \frac{1}{C_{eq}^1} \rightarrow C_{eq}^2 = \frac{C_1 C_{eq}^1}{C_1 + C_{eq}^1}$$

- Finally, add up capacitors in parallel:
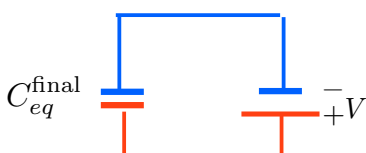
$$C_{eq}^{final} = C_2 + C_{eq}^2 = C_2 + \frac{C_1 C_{eq}^1}{C_1 + C_{eq}^1}$$




$$C_{eq}^{final} = C_2 + \frac{C_1 (C_3 + C_4)}{C_1 + C_3 + C_4}$$

106

- Equations for equivalent capacitance become quite complicated fast
- If your given numbers for the capacitance use them for simplification!


Ex. Simplifying Capacitors II:

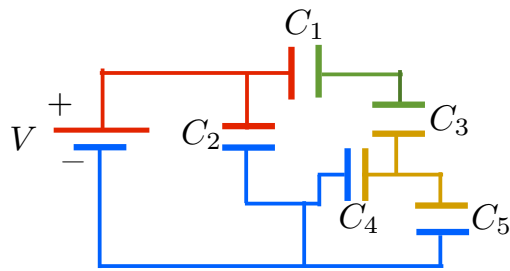

$$\begin{aligned} C_1 &= 3.0 \text{ nF} & C_2 &= 2.1 \text{ nF} \\ C_3 &= 2.0 \text{ nF} & C_4 &= 4.7 \text{ nF} \\ C_5 &= 1.3 \text{ nF} \end{aligned}$$

- Lets use color to find the capacitors in series and parallel.
 - Entire voltage V across C_2 -> everything is in parallel to C_2
 - Voltage across C_4 and C_5 is the same (yellow -> blue) thus they are in parallel.
 - Voltage across C_1 and C_3 are different so they are in series.
- Do C_4 & C_5 first: $\tilde{C}_{eq}^1 = C_4 + C_5 = 6 \text{ nF}$

- Redraw circuit

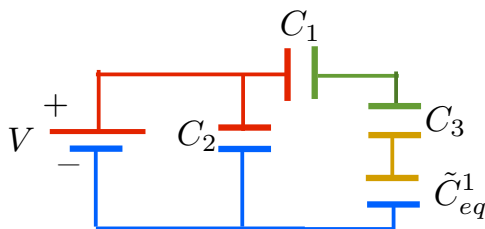


$$\tilde{C}_{eq}^1 = 6 \text{ nF}$$

- Now C_1 , C_3 , and \tilde{C}_{eq}^1 are in series and we must calculate those before doing C_2 .

$$\frac{1}{\tilde{C}_{eq}^2} = \frac{1}{C_1} + \frac{1}{C_3} + \frac{1}{\tilde{C}_{eq}^1} = \frac{1}{3 \text{ nF}} + \frac{1}{2 \text{ nF}} + \frac{1}{6 \text{ nF}} = \frac{1}{1 \text{ nF}}$$

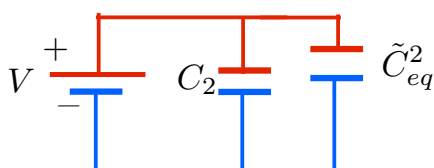- Redraw circuit: $\tilde{C}_{eq}^2 = 1 \text{ nF}$




- Total capacitance is now just sum over last two:

$$\tilde{C}_{eq}^{\text{total}} = C_2 + \tilde{C}_{eq}^2 = 2.1 \text{ nF} + 1 \text{ nF} = \boxed{3.1 \text{ nF}}$$

Dielectrics:

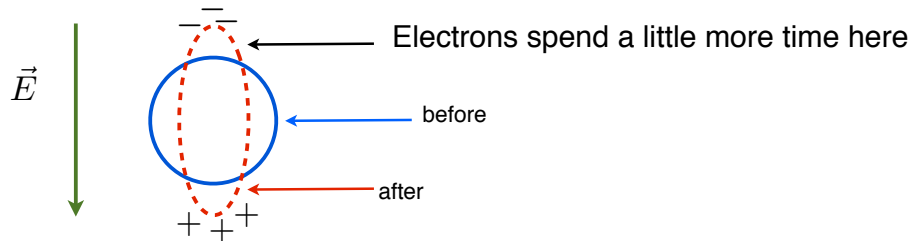
- E -fields can induce dipoles in insulating materials
- Recall that electrons are not free to move in an insulator
- Suppose I apply an E-field to a round atom or molecule



- This is a result of induction and is called **Polarization**
- Materials that behave like dipoles under E-fields are called **dielectrics**


109

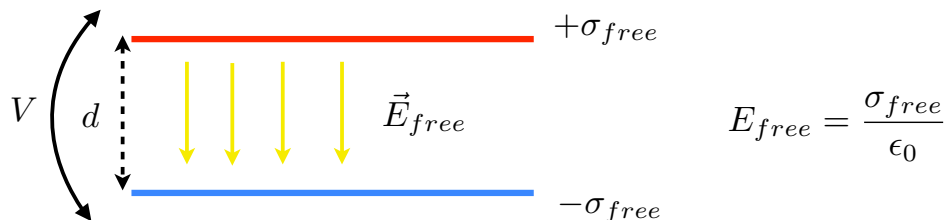- Suppose I have two charged plates, charged by a voltage source V:



- Now I remove V, and add a dielectric inside:

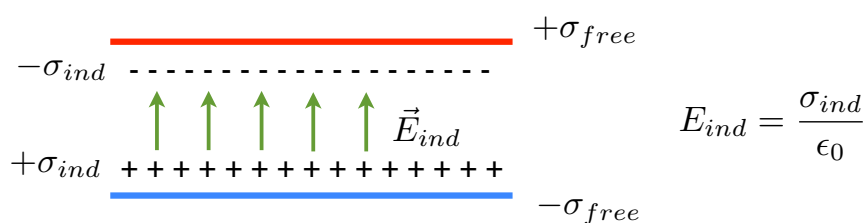- Negative charges of dielectric go toward positive plate; positive charges toward negative plate



- Dipoles create constant E-field in opposite direction from \vec{E}_{free}

110

- The total electric field inside the plates is just the vectorial sum of the 2 fields:

$$\vec{E}_{total} = \vec{E}_{free} + \vec{E}_{ind}$$

- Since E_{ind} is in opposite direction, the total magnitude of the E-field is:

$$|E_{total}| = |E_{free}| - |E_{ind}|$$

← since opposite direction

- The induced charge can never be as large as the free charge so we assume:

$$\sigma_{ind} = \beta \sigma_{free} \quad \beta \ll 1 \quad \longrightarrow \quad E_{ind} = \frac{\beta \sigma_{free}}{\epsilon_0}$$

- Therefore, the total E-field is now: $E_{total} = E_{free} - \beta E_{free} = (1 - \beta) E_{free} = 1/\kappa$

- κ is called the “**dielectric constant**”.

- The total electric field inside the capacitor will therefore always be:

$$\vec{E} = \frac{\vec{E}_{free}}{\kappa}$$

111

- We can also write the E-field inside the capacitor as:

$$E = \frac{1}{\kappa} E_{free} = \frac{\sigma_{free}}{\kappa \epsilon_0} = \frac{\sigma_{free}}{\epsilon}$$

where $\epsilon = \kappa \epsilon_0$ is called the “**electric permittivity**” of the dielectric.

← permittivity of free space

- > can just replace ϵ_0 with ϵ .

- Sample dielectric constant values:

Vacuum	1.0
Air	1.000059 (always assumed to be = 1)
Paper	3
Glass	5

- Some materials are dipoles even without an E-field, these permanent dipoles can be extremely strong:


Water	80.4
-------	------

112

- What does a dielectric do to the capacitance?

$$\uparrow C = \frac{Q}{V} = \frac{Q}{\downarrow Ed}$$

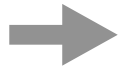- Dielectrics always decrease the E-field -> Capacitance always increases.



Using a dielectric allows me to store more charge on capacitor

- The capacitance with a dielectric can be expressed as:

$$C_{\kappa} = \frac{Q}{V} = \frac{Q}{E_{total}d} = \frac{\kappa Q}{E_{free}d} = \kappa \frac{Q}{E_{free}d} = \kappa C$$


- Capacitance is just κ times the capacitance without the dielectric

$$C_{\kappa} = \kappa C$$

113

Ex. Dielectrics I:

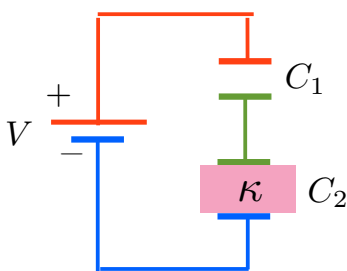- Suppose I have two capacitors C_1 and C_2 with same area A and separation d , and C_2 is filled with a dielectric with constant κ



- a) What is the charge on each capacitor?**

- Recall that the charge on each capacitor in series is the same

$$Q = C_{eq}^{series} V$$

- Must find equivalent capacitance:

$$\frac{1}{C_{eq}^{series}} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{C_1} + \frac{1}{\kappa C_1} \rightarrow C_{eq}^{series} = \frac{\kappa C_1}{\kappa + 1}$$

- Therefore: $Q = \frac{\kappa C_1}{\kappa + 1} V$ but $C_1 = \frac{\epsilon_0 A}{d}$

$$Q = \frac{\epsilon_0 A}{d} \frac{\kappa}{\kappa + 1} V$$

- b) What is the total energy inside the capacitors?**

$$U = \frac{1}{2} QV \text{ but since we know total charge: } Q = C_{eq} V$$

$$U = \frac{1}{2} C_{eq} V^2 = \frac{1}{2} \frac{\kappa C_1}{\kappa + 1} V^2 = \frac{\epsilon_0 A}{2d} \frac{\kappa}{\kappa + 1} V^2$$

114


c) What is the E-field inside C2?

- Recall for E-field in capacitor with dielectric: $E = \frac{1}{\kappa} E_{free} = \frac{\sigma}{\kappa \epsilon_0} = \frac{Q}{\kappa \epsilon_0 A}$

- We have already calculated charge though all capacitors: $Q = \frac{\epsilon_0 A}{d} \frac{\kappa}{\kappa + 1} V$

Therefore: $E = \frac{1}{\kappa \epsilon_0 A} \frac{\epsilon_0 A}{d} \frac{\kappa}{\kappa + 1} V = \boxed{\frac{V}{d} \frac{1}{\kappa + 1}}$

Ex. Dielectrics II:

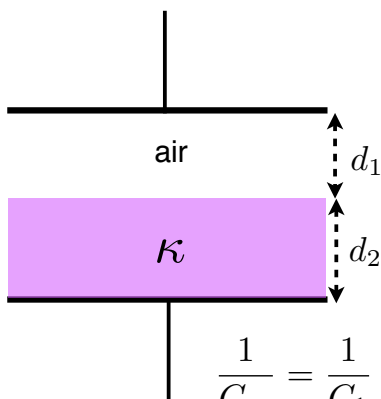

- Suppose I am given the following capacitor with area A. What is the capacitance?

- This looks like two capacitors in series, one with no dielectric, one with dielectric

$$C_1 = \frac{\epsilon_0 A}{d_1} \quad C_2 = \kappa \frac{\epsilon_0 A}{d_2}$$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{d_1}{\epsilon_0 A} + \frac{d_2}{\kappa \epsilon_0 A} = \frac{\kappa d_1 + d_2}{\kappa \epsilon_0 A}$$

$$\boxed{C_{eq} = \frac{\kappa \epsilon_0 A}{\kappa d_1 + d_2}}$$