

# Current and Resistors

116

- So far we have discussed a lot about charges, but have not talked much about how they move.


- The key quantity needed in the description of charge motion is the **Electric Current**:

$$I = \frac{dq}{dt} \quad \rightarrow \quad q(t) = \int_0^t I(t') dt' \quad I = [A = \frac{C}{\text{sec}}]$$

- In this chapter we will discuss currents that move in a single direction only, these are called **direct currents**, and are the currents produced in batteries, and used in cars, computers,....

- Currents are generated in conductors since charges can move.

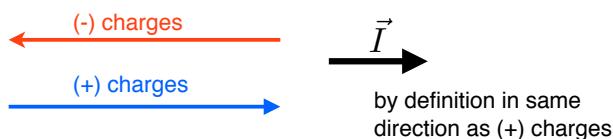- It is the electrons that move in a conductor, but in physics we define the charge to be in the direction that positive charges move. (because \$100 guy got it wrong)



- Although electrons move, can always think of (+) charges as moving in opposite direction

117

- If we apply a potential difference across a conductor, then an E-field is created inside the conductor
- As in any conductor, the electrons try to move around until they cancel the E-field
- However, if the potential (E-field) is constant, than the electrons can never cancel the E-field and they will keep moving around
- Therefore, there is a relationship between the current (charges moving) and the applied voltage.
- Often times there is a linear relationship between current and potential: we call this **Ohm's "Law"**
- Here we will do a simple derivation of Ohm's law since the full version requires quantum mechanics.
- Suppose I have a Cu wire at 300K, then the electron velocity is:  $v_e \approx 10^6$  m/s
- The time it takes before an electron bumps into a Cu atom is called the **mean free-path**

$$\tau \approx 10^{-14} \text{ sec}$$

118

- Also, I can calculate the number of free electrons per m^3 in Cu:  $n \approx 10^{29}$  1/m<sup>3</sup>
- Now suppose we apply a voltage across our Cu wire:



$$F = eE$$

(I am only worried about magnitudes here  
so forget the minus sign at the moment)

- We also know that F=ma, so:  $a = \frac{F}{m_e}$    $v_d = a\tau = \frac{eE}{m_e}\tau$  (**drift velocity**)
- The drift velocity tells us how fast the electrons move due to the E-field.

If  $E \uparrow$  then  $V_d \uparrow$  and if  $\tau \uparrow$  then  $V_d \uparrow$


- Consider a 10m Cu wire with potential difference V=10V  $\rightarrow E=1$  V/m

$$\text{in this case: } v_d = \frac{1.6 \times 10^{-19} \text{ C} \cdot 3 \times 10^{-14}}{10^{-30} \text{ kg}} \approx 5 \times 10^{-3} \text{ m/s}$$

- Electrons move 10 billion times faster due to thermal motion compared to the E-field.
- In fact, a turtle moves faster than the electrons!

119

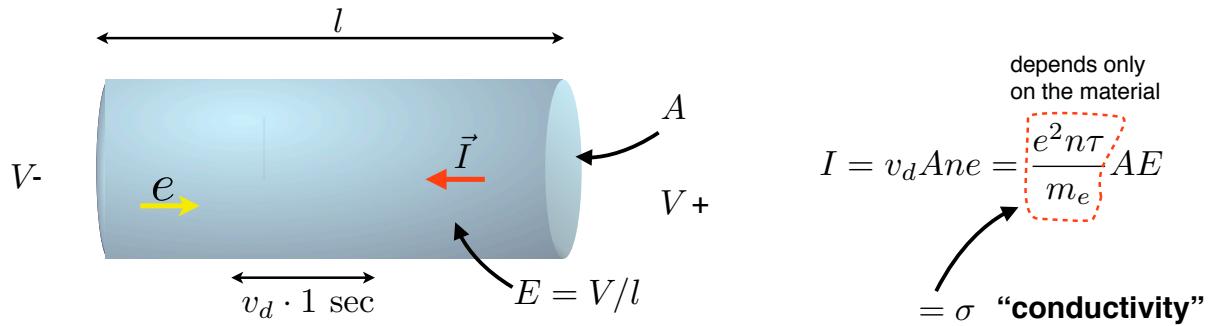- Lets now calculate the current through a conductor:



- ex. Cu @ 300K:  $\sigma \approx 10^8$

- Can rearrange to solve for potential and define resistance:

$$I = \sigma A \frac{V}{l} \quad \rightarrow \quad V = \frac{l}{\sigma A} I = RI \quad R = \frac{l}{\sigma A} \quad \text{"resistance"}$$

- Can also define the "resistivity":  $\rho = 1/\sigma$

- We now have **Ohm's Law**:

$$\boxed{V = IR} \quad \text{with} \quad R = \frac{l}{\sigma A} = \frac{l \rho}{A} \quad [\Omega] \quad (\text{Ohm})$$


120

- We see that resistance is proportional to length, inversely proportional to area

- Think of current as flowing water, bigger pipe means easier flow; longer pipe more resistance

- Ohm's law also works for many insulators

- Suppose I am given a wire:

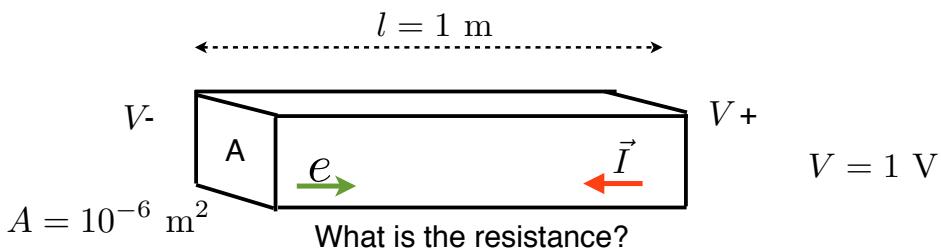

- We know l and A, so only need  $\sigma$

- For good conductors, Au, Ag, Cu:  $\sigma \approx 10^8 \rightarrow \rho = 10^{-8} \quad R = 10^6 \rho = 10^{-2} \Omega$

- For good insulators, Glass, quartz:  $\sigma \approx 10^{-12} - 10^{-16} \rightarrow \rho = 10^{12} - 10^{16}$



assuming  $\rho = 10^{14} \rightarrow R = 10^{20} \Omega$  Huge resistance

121

- We can use Ohm's law to get the current:

$$I_{\text{Cu}} = 100 \text{ A} ; I_{\text{Glass}} = 10^{-20} \text{ A}$$

- Suppose I have the following circuit:

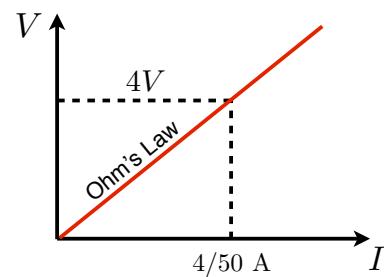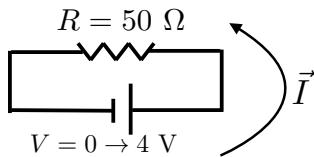


- Conductivity  $\sigma$  is a strong function of temperature:

- higher temperature  $\rightarrow$  higher resistance

- Ohm's law does not hold very well in general

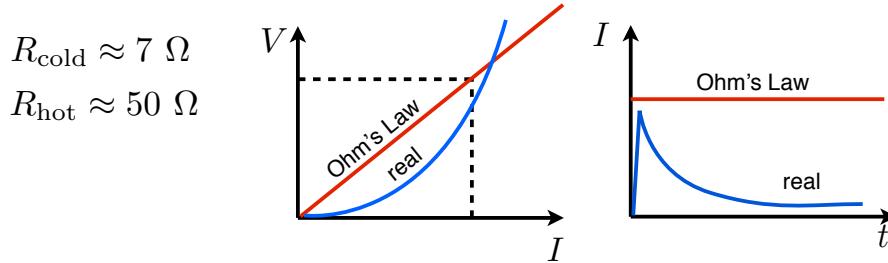
Light bulbs: light bulbs get hotter as current flows, this is why they glow!



122

### Circuits of Resistors:

#### Resistors in series:

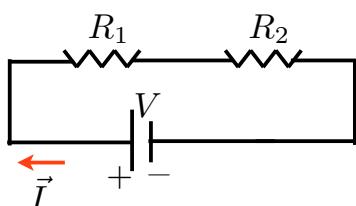

- Current through each resistor is the same

- Think of water through a pipe: "what goes in must come out"

$$V_1 = IR_1 \quad V_2 = IR_2$$


- We know that the total potential  $V = V_1 + V_2$ :

$$V = V_1 + V_2 = IR_1 + IR_2 = I(R_1 + R_2) = IR_{\text{eq}}$$

- For resistors in series:  $R_{\text{eq}}^{\text{series}} = \sum R_i^{\text{series}}$

123

### Resistors in parallel:

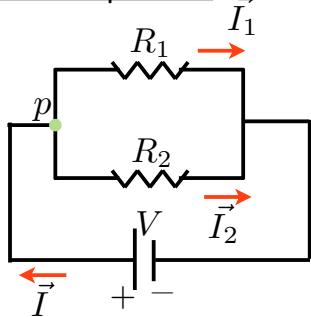

- At point P, the current splits into two components:

$$I = I_1 + I_2$$

- Like capacitors in parallel, the potential across both resistors is the same

$$V = I_1 R_1 \quad V = I_2 R_2$$

- Can evaluate the total current in the circuit:

$$I = I_1 + I_2 = \frac{V}{R_1} + \frac{V}{R_2} = V \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{V}{R_{eq}}$$

- For resistors in parallel:


$$\frac{1}{R_{eq}} = \sum \frac{1}{R_i}$$

- Can always combine resistors in series or parallel into a single resistor

124
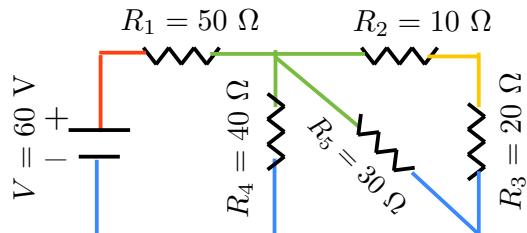
### Ex. Simplifying resistors:

- What is the equivalent resistance of the 5 resistors?



- Use color for potentials (as before)

->  $R_4$  &  $R_5$  in parallel

->  $R_2$  &  $R_3$  in series

-  $R_5$  is connected in the middle of  $R_1, R_2$  &  $R_4$


-> we cannot combine  $R_1$  and  $R_4$ , or  $R_1$  and  $R_2$  yet

- Start with  $R_2$  and  $R_3$  (or  $R_4$  and  $R_5$ ):  $R_{eq}^{series} = R_2 + R_3 = 30 \Omega$

- Now do  $R_4$  and  $R_5$ :  $\frac{1}{R_{eq}^{para}} = \frac{1}{R_4} + \frac{1}{R_5} = \frac{1}{120} \rightarrow R_{eq}^{para} = \frac{120}{7} \Omega$

125


- Redraw the circuit:

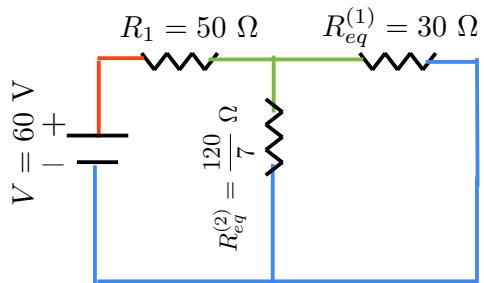

- Now  $R_{eq}^{(1)}$  and  $R_{eq}^{(2)}$  are in parallel, do them next:

$$\frac{1}{R_{eq}^{(3)}} = \frac{1}{R_{eq}^{(1)}} + \frac{1}{R_{eq}^{(2)}} = \frac{1}{30} + \frac{7}{120} = \frac{11}{120} \rightarrow R_{eq}^{(3)} = \frac{120}{11} \Omega$$

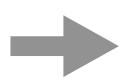- We are left with  $R_1$  in series with  $R_{eq}^{(3)}$



$$R_{eq}^{\text{total}} = R_1 + R_{eq}^{(3)} = 50 \Omega + \frac{120}{11} \Omega = \boxed{\frac{670}{11} \Omega}$$