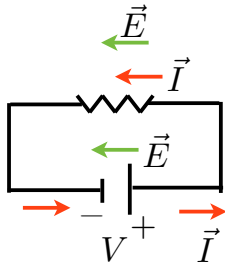


- Consider the following circuit:



- Lets follow the current around and draw the E-field across the circuit elements

- The E-field points in the opposite direction from the current inside the voltage source!

- Something must supply energy so that the (+) charges can go from low \rightarrow high potential

- Like gravity: "A ball cannot go uphill without some push"

- Work must be done on the charges, the energy must come from somewhere.


- In a battery, the work comes from chemical reactions

- In a power plant, the work comes from the mechanical energy generated from steam.

127

EMF:

- Suppose $R = \infty$, and thus $I = 0$

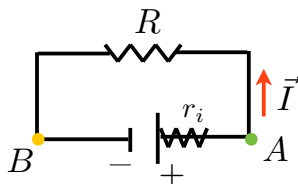

$$V_A - V_B = V_b = \mathcal{E}$$

"EMF"

- EMF is the potential across a fixed voltage source when no current is flowing

- Suppose $R \neq 0$, therefore $I > 0$


- The voltage source always has some small internal resistance r_i



$$\mathcal{E} = I(R + r_i) \quad V_b = IR = \mathcal{E} - Ir_i$$

-If $R=0$ then you get maximum current in circuit: $I_{\max} = \frac{\mathcal{E}}{r_i} \rightarrow V_b = 0$

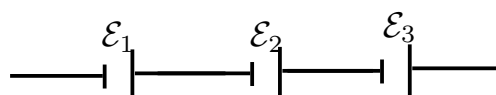
-For batteries in series: $\mathcal{E}_{\text{total}} = \mathcal{E}_1 + \mathcal{E}_2 + \mathcal{E}_3$



128

Power:

- Suppose: $V_A > V_B$

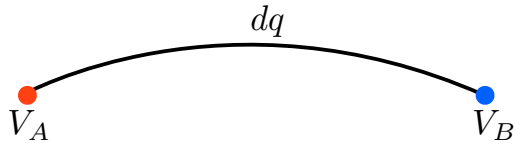

- Let me move a charge dq from V_A to V_B -> requires me to do work:

$$dW = dq (V_A - V_B)$$

- divide both sides by dt : $\frac{dW}{dt} = \frac{dq}{dt} (V_A - V_B)$

\swarrow
 I

- Now have work/unit time = “**Power**” : $P = IV$ $\left[\frac{J}{s} = W \right]$ (always holds)

- If Ohm’s Law holds then $V = IR$:

$$P = I^2 R = V^2 / R \quad (\text{ONLY WHEN OHM’S LAW IS VALID})$$

129



- Assuming an Ohmic resistor: $P = I^2 R$

$$I = 1 \text{ A}, \quad R = 100 \, \Omega \quad \rightarrow P = 100 \text{ W}$$

$$I = 2 \text{ A}, \quad R = 100 \, \Omega \quad \rightarrow P = 400 \text{ W}$$

- This energy is dissipated as heat

- If the resistor gets hot enough, you can get light (i.e. a lightbulb)

- Tungsten filament in a lightbulb $\approx 2500 \text{ K}$

ex light blub:

- Assume: $P = 100 \text{ W}$ $V = 220 \text{ V}$

- Using $P = IV$: $I = 0.45 \text{ A}$

- Using $V = IR$: $R = 489 \, \Omega$

- If $V=110\text{V}$ then $I=0.9\text{A}$. This is why we use 220V in Korea; less current = smaller wires.

- The human body generated $\sim 100\text{W}$. We do not get too hot since we have large surface area.

130

ex shorted battery:

- If I look at the total power generated in a resistor + the battery then:

$$P = I\mathcal{E} = I^2 (R + r_i)$$

- If $R=0$ (by shorting the battery):

$$I_{\max} = \frac{\mathcal{E}}{r_i} \quad \longrightarrow \quad P_{\max} = \frac{\mathcal{E}^2}{r_i} = I_{\max}^2 r_i$$

- Consider a shorted 9V battery:

$$\mathcal{E} = 9 \text{ V} \quad r_i = 2 \Omega \quad \rightarrow \quad I_{\max} \approx 4.5 \text{ A}$$

$$\longrightarrow P_{\max} = 40 \text{ W}$$

- All 40W will turn into heat -> battery will get hot.
- For 9V battery not so bad, but car battery this is very dangerous: $P_{\max} = 7000 \text{ W}$



131

- So far we have only talked about electrons moving as current

- However, currents can also be formed by ions; atoms with extra, or missing, electrons


- This is how every battery works

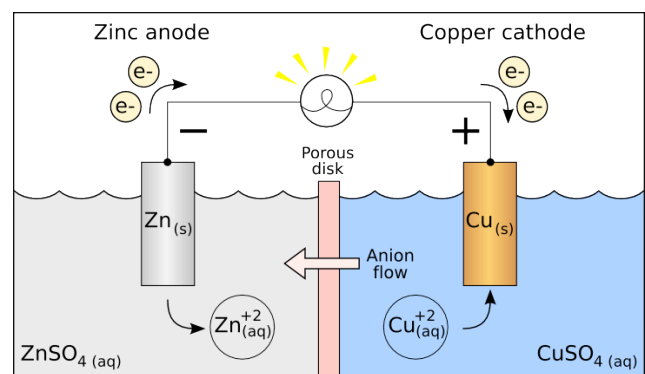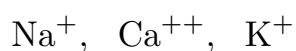- Electric currents in the human body are also generated by moving ions:




Zinc-Copper Battery

Structure of a Skeletal Muscle

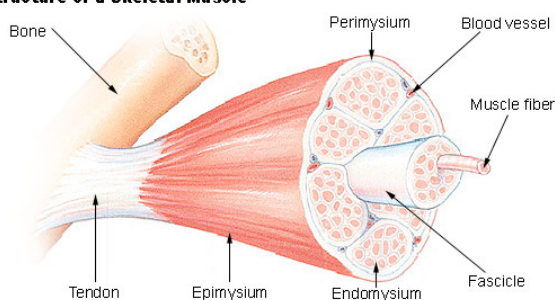

Muscle Cells

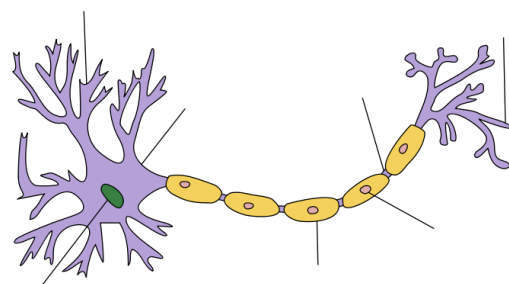


Neuron

132


- Salt water is a very good source of ions:

- In water, salt breaks into ions:

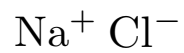

- These ions increase the conductivity of water by 1 million times

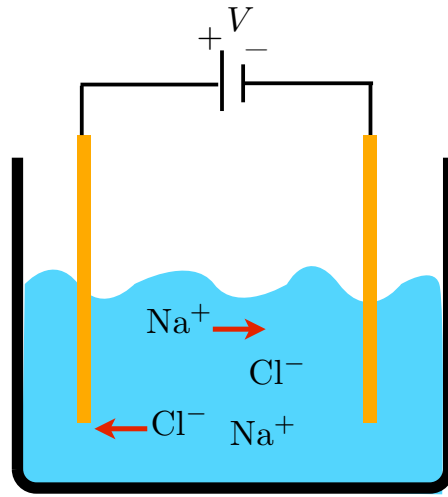- If I apply a voltage between two metal plates in salt water, the ions will move generating a current



Pickle Demo